

Name: \_\_\_\_\_

Block: \_\_\_\_\_




Science 9  
Wolfe, Spring 2019

**Phet Circuits Intro**  
**(adapted from Clarke Phet Circuits Lab, Briana Clarke at Envision Academy)**

1. Type "PhET html Circuit intro" to find and run lab.

Notice: A circuit is a path, like a circle, whose start and end are at the same place.

- a. Complete the circuits below by drawing the missing element.
- b. Write observation about electrons

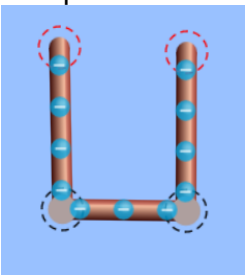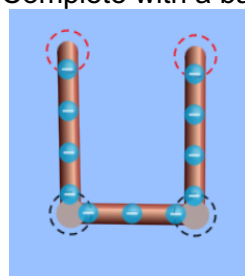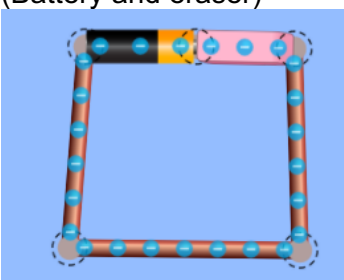Drawing	Observations about electrons
<p>Complete with a wire</p> 	
<p>Complete with a battery</p> 	
<p>(Battery and eraser)</p> 	

Notice: Current is the movement of electrons; it is measured at a rate through which electrons pass a certain point, like a battery, per second. The faster the electrons move, the higher the current.

2. Was there current for the circuit with the eraser? \_\_\_\_\_


Was there current for the circuit with just the wire? \_\_\_\_\_

3. Materials that are good at letting electricity through are called conductors. Try each item and see which let electricity flow easily and which slow or stop it.

Good conductors: \_\_\_\_\_

Poor conductors: \_\_\_\_\_

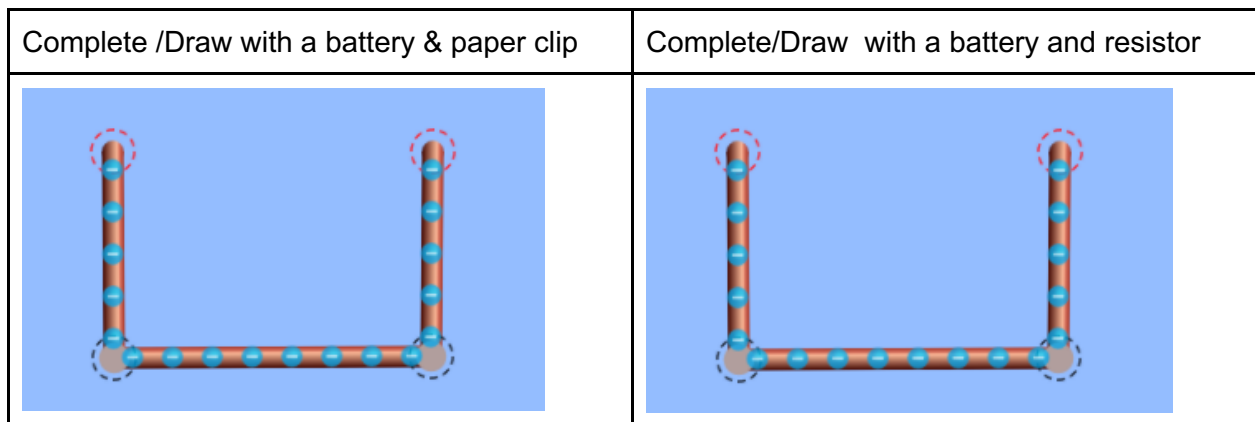Batteries, like the ones in a tv remote controller, provide voltage. That voltage is pressure force that gives electrons the potential energy to move through a circuit.



4. Compare the difference in current between the 2 pictures.

---

---

5. What does the resistor do to the electrons/current?

---

---




6. What do you think the resistor's purpose is?

---

---

Create 3 separate circuits side by side.

7. Draw circuits below with **light rays** for each scenario to represent “brightness.” Label speeds of currents “slow, medium, and fast” and Label light bulbs “dim, medium, bright”

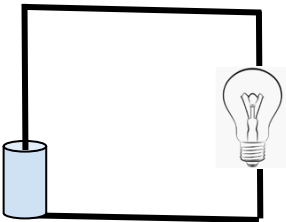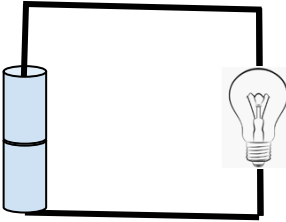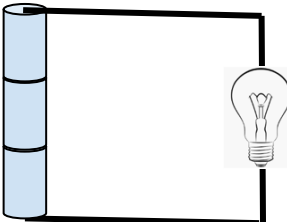1 battery, 1 light bulb, wires	2 batteries, 1 light bulb, wires	3 batteries, 1 light bulb, wires
		

8. What happened to the current (speed of electrons) as the number of batteries increased?

---



---

9. What happened to the bulb’s brightness as the number of batteries increased?




---



---

Create 3 separate circuits side by side.

10. Draw circuits below with **light rays** for each scenario to represent “brightness.” Label speeds of currents “slow, medium, and fast” and Label light bulbs “dim, medium, bright”

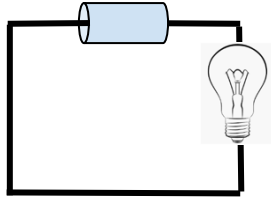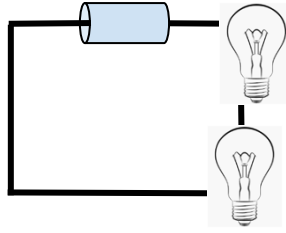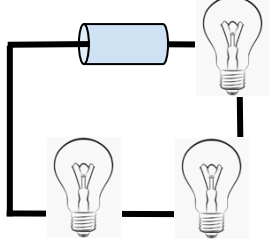1 battery, 1 light bulb	1 battery, 2 light bulbs	1 battery, 3 light bulbs
		

11. What happened to the current as the number of light bulbs increased?

---

---

12. What happened to the bulbs' brightness as the number of bulbs increased?

---

---

13. Try to think about how questions 11 and 12 are related. Give a theory to explain.

---

---

---

---

14. Remember what a resistor does. (Check Q&A 5). What do a resistor and a light bulb have in common?

---

---